

Figure 1.1 Arduino Uno board with important components

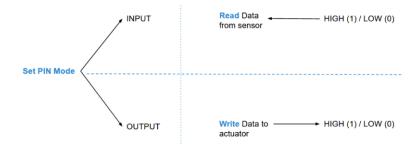


Figure 1.2 Input and output mode of digital pin

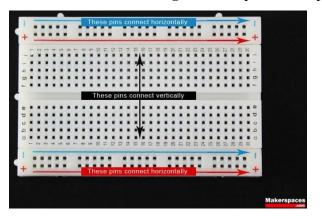


Figure 1.3 Breadboard internal pins connection

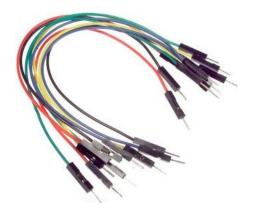


Figure 1.4 Jumper wire



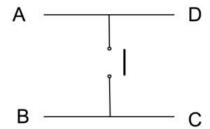


Figure 1.5 Push button switch internal pin connection

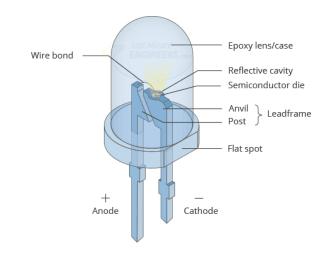


Figure 1.6 LED Schematic

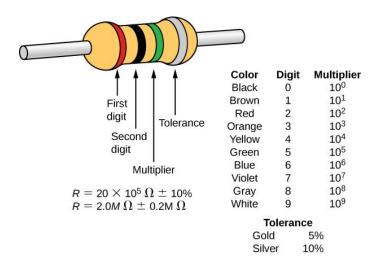


Figure 1.7 Resistor and Its color code

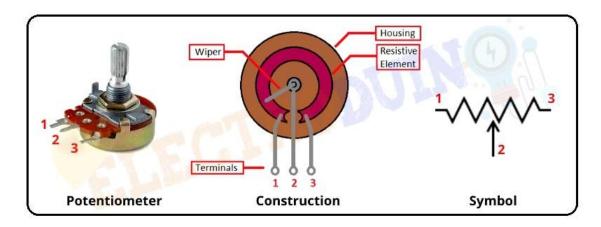


Figure 1.8 Potentiometer and its pin schematic

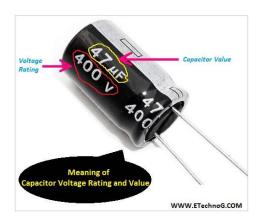


Figure 1.9 Capacitor shown with value and ratings

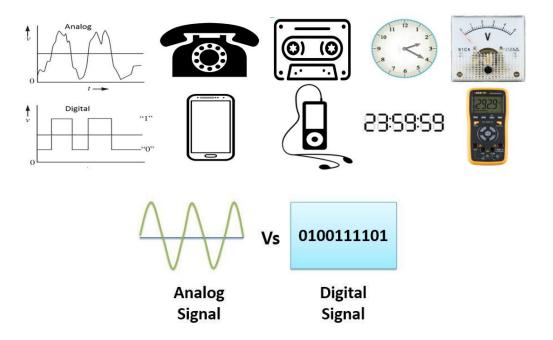


Figure 1.10 Analog and digital signal, device and difference

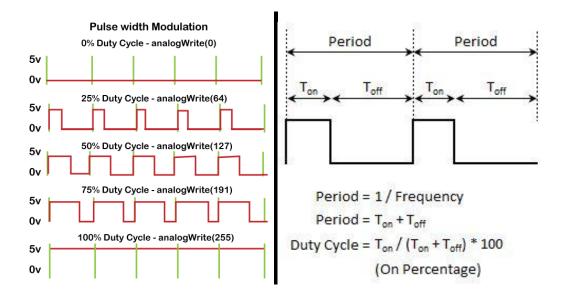


Figure 1.11 PWM and duty cycle calculation

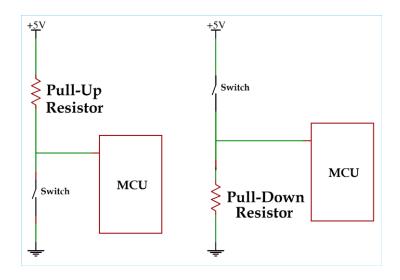


Figure 1.12 Pull up and pull down resistor connection

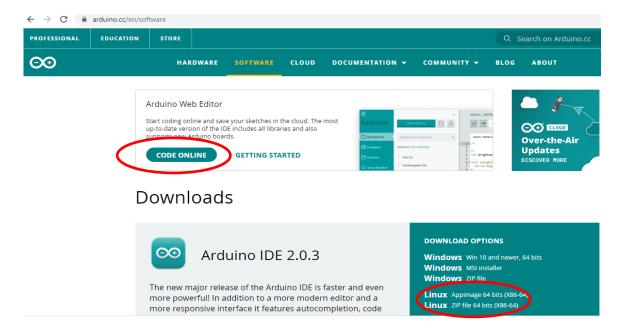


Figure 2.1 Arduino software downloading option

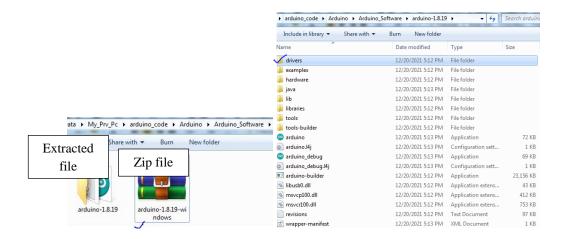


Figure 2.2 Arduino software zip with application and driver

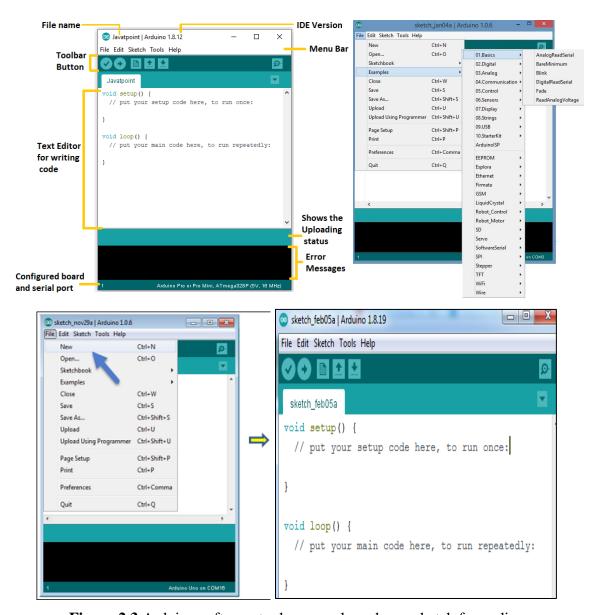


Figure 2.3 Arduino software tools, example and new sketch for coding

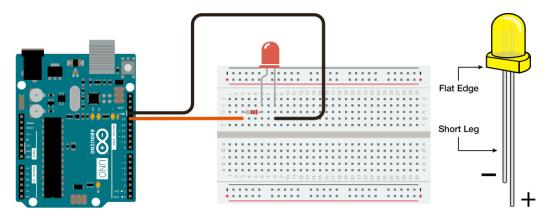


Figure 3.1 Circuit diagram for LED blinking

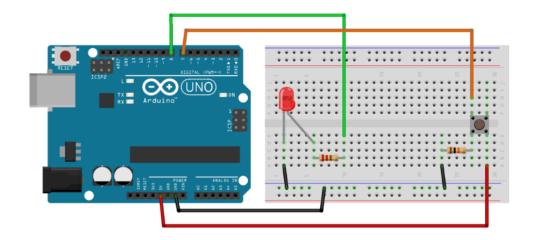


Figure 4.1 Arduino circuit diagram for led blink using external pull down resistor

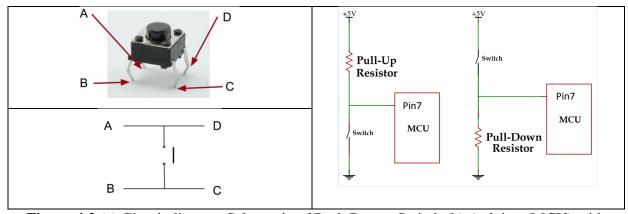


Figure 4.2 (a) Circuit diagram Schematic of Push Button Switch (b) Arduino (MCU) with external pull down resistor (https://roboticsbackend.com/arduino-input pullup-pinmode/)

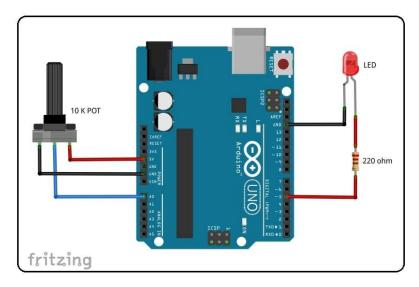


Figure 5.1 Circuit Diagram for LED Brightness Control using Potentiometer (https://www.electroduino.com/led-brightness-control-using-potentiometer/)

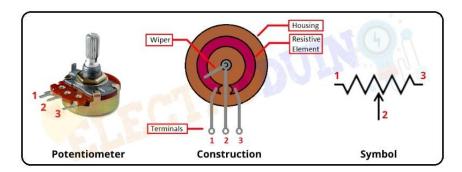


Figure 5.2 Potentiometer internal construction and symbol

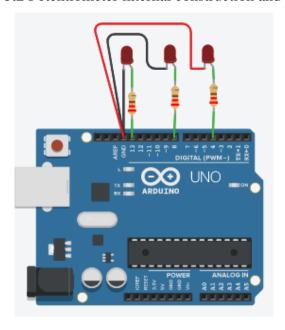


Figure 6.1 Circuit Diagram for blinking multiple LED at same time

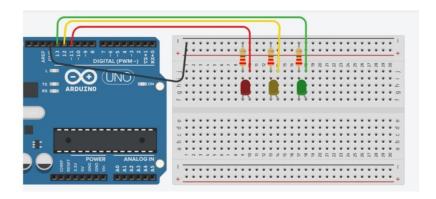


Figure 7.1 Circuit Diagram for scrolling RGB LEDs

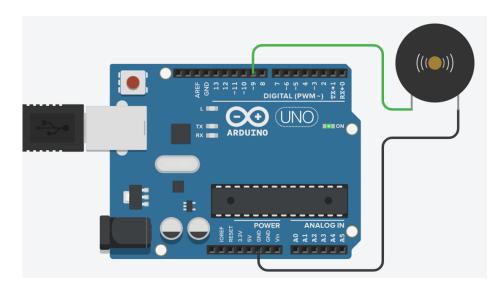


Figure 8.1 Circuit Diagram for Piezo buzzer (https://www.electrovigyan.com/arduino/piezo-buzzer/)

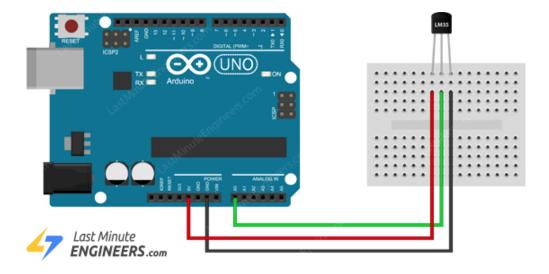


Figure 9.1 Circuit Diagram for temperature sensor using LM35

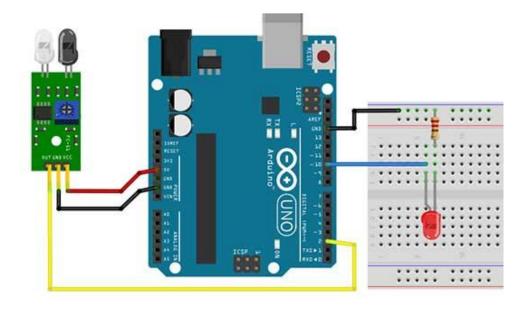


Figure 10.1 Circuit Diagram for Obstacle Avoidance Sensor using Infrared IR Sensor

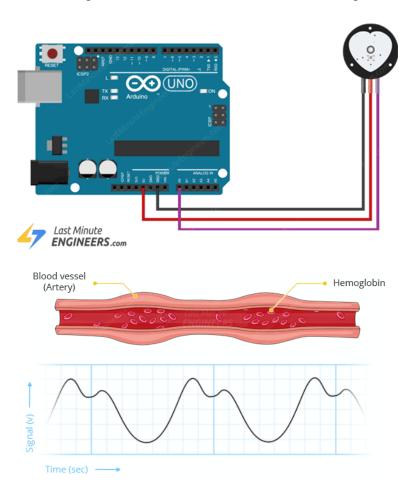


Figure 11.1 Circuit diagram for Arduino heart beat send and its working principle

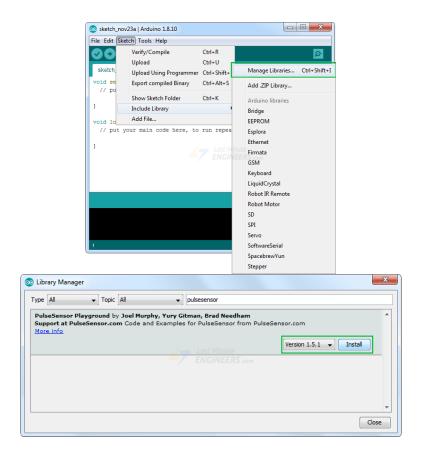


Figure 11.2 Library Installation

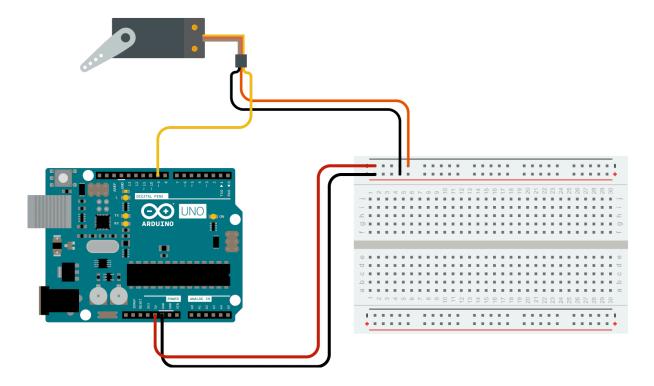


Figure 12.1 Circuit diagram for servo back and forth range of motion

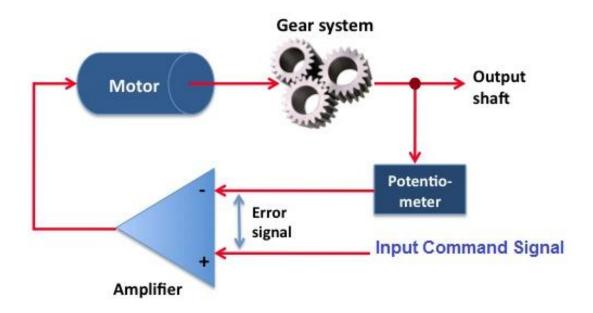


Figure 13.1 Servo motor and its mechanism

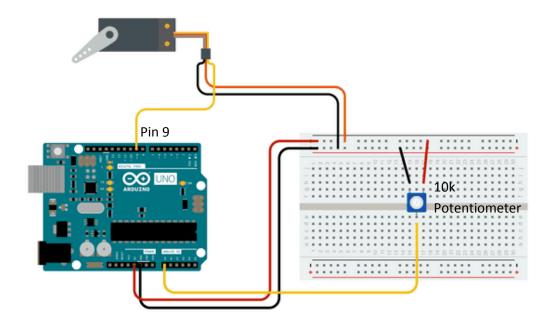


Figure 13.2 Circuit diagram for servo motor control with Arduino

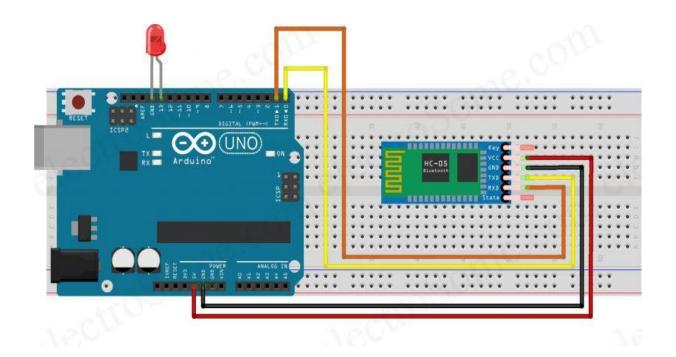


Figure 14.1 Circuit diagram for Bluetooth module with Arduino



Figure 15.1 Circuit diagram for LCD display